



DU-003-003207

Seat No. _____

B. C. A. (Sem. - II) (CBCS) Examination

April / May - 2015

CS - 09 Comp. Organization & Architecture (New)

Faculty Code : 003

Subject Code : 003207

Time : $2\frac{1}{2}$ Hours]

[Total Marks :70

Instruction : (1) There are three Questions and all Questions are compulsory.

(2) Answer of MCQ and All Questions must be written in answer sheet only

Section - I

Q:1 Multiple Choice Questions :

[20]

1. An inverter is also called a _____ gate.

(A) NAND

(B) AND

(C) NOT

(D) NOR

2. How many full-adders are required to construct an m-bit parallel adder ?

(A) m-1

(B) m+1

(C) m

(D) m/2

3. A demultiplexer is also known as _____

(A) encoder

(B) multiplexer

(C) data selector

(D) data distributor

4. Digital design often starts by constructing a _____ table.

(A) two-stage

(B) truth table

(C) standard

(D) None

DU-003-003207]

1

[Contd...

5. _____ has become the most widely used bipolar family.
- (A) DTL (B) TTL
(C) ECL (D) MOS
6. Binary coded decimal (BCD) number express each digit as a _____
- (A) byte (B) nibble
(C) bit (D) All of the above
7. The hexadecimal number system is widely used in analyzing and programming _____
- (A) registers (B) vacuum tube
(C) chips (D) microprocessors
8. Software interrupt is initiated by _____
- (A) signals (B) wave form
(C) executing an instruction (D) none
9. Which Bus is bi-directional ?
- (A) Address Bus (B) Control Bus
(C) Duty Bus (D) None
10. Which is not stack operation?
- (A) PUSH (B) POP
(C) PULL (D) PEEP
11. Which of following electronic component is not found in ordinary ICs ?
- (A) diodes (B) resistors
(C) transistor (D) inductors
12. What is reverse polish notation of $A + B * C + D$?
- (A) $ABC * D++$ (B) $ABCD * ++$
(C) $A * BCD++$ (D) None
13. A gate is a logic circuit with one or more input signals but _____ output signal.
- (A) one (B) two
(C) double (D) more than one

14. Which of following flip-flops is free from race around problem ?

- (A) T flip-flop (B) SR flip-flop
(C) master-slave JK (D) None

15. A shift register can be used for

- (A) parallel to serial conversion (B) serial to parallel conversion
(C) digital delay line (D) All of above

16. A flip-flop can store _____

- (A) 1 bit of duty (B) 2 bit of duty
(C) 3 bit of duty (D) 4 bit of duty

17. Which of the following is not a type of Interrupts ?

- (A) External Interrupts (B) Internal Interrupts
(C) Software Interrupts (D) Analog Interrupts

18. Parallel adders are _____

- (A) Combinational logic circuits (B) Sequential logic circuits
(C) Both of above (D) All of the above

19. DMA stands for _____

- (A) Direct memory alternation (B) Direct memory access
(C) Direct module (D) None

20. An OR gate has 6 inputs , how many words are in its truth table ?

- (A) 64 (B) 32
(C) 16 (D) 128

Section - II

Q : 2 (A) Attempt the following : (Any three) [6]

1. Discuss NAND gate as a universal gate.
2. Explain SR Flip-Flop.
3. Explain Half Subtractor.
4. What is the difference between Half Adder and Full Adder.

5. Write a short note on modes of data transfer.
6. Explain parity bit.

(B) Attempt the following : (Any three) [9]

1. Write a short note on counter.
2. Explain Input output processor.
3. Explain Shift Register.
4. Write note on control word.
5. Write note on Encoder.
6. What is Interrupt ? Explain types of Interrupt.

(C) Attempt the following : (Any two) [10]

- 1 Explain Stack Organization.
2. Explain Master slave Flip-Flop.
3. Explain Polish Notation with its advantages.
4. Explain general register organization.
5. Explain register with parallel load.

Q: 3 (A) Attempt the following : (Any three) [6]

1. Define : Address Bus , Data Bus , Control Lines
2. Explain Micro operation.
3. Explain LSI , MSI , SSI.
4. Explain decoder.
5. What is logic gate ? Explain logic gates with truth table.
6. Convert into reverse polish notation.

$$(A*B)/[(C*D)+E*F]$$

(B) Attempt the following : (Any three) [9]

1. Explain Hexa Decimal Number System.
2. Write a short note on asynchronous serial transfer.
3. Write a short note on DMA transfer.
4. Write a short note on unidirectional shift register.
5. Explain D Flip-Flop.
6. Write a note on Ripple Counter.

(C) Attempt the following : (Any two) [10]

1. What is combinational circuit ? Explain with types.
2. What is Flip Flop ? Explain with types.
3. Prove following Boolean algebra.
 (a) $AB + A(B+C)+B(B+C)=B+AC$
 (b) $(X+Y')(X'+Y) = XY + X'Y'$
4. Write note on Error Detection Code.
5. Explain Asynchronous 4 bit Binary Counter.